
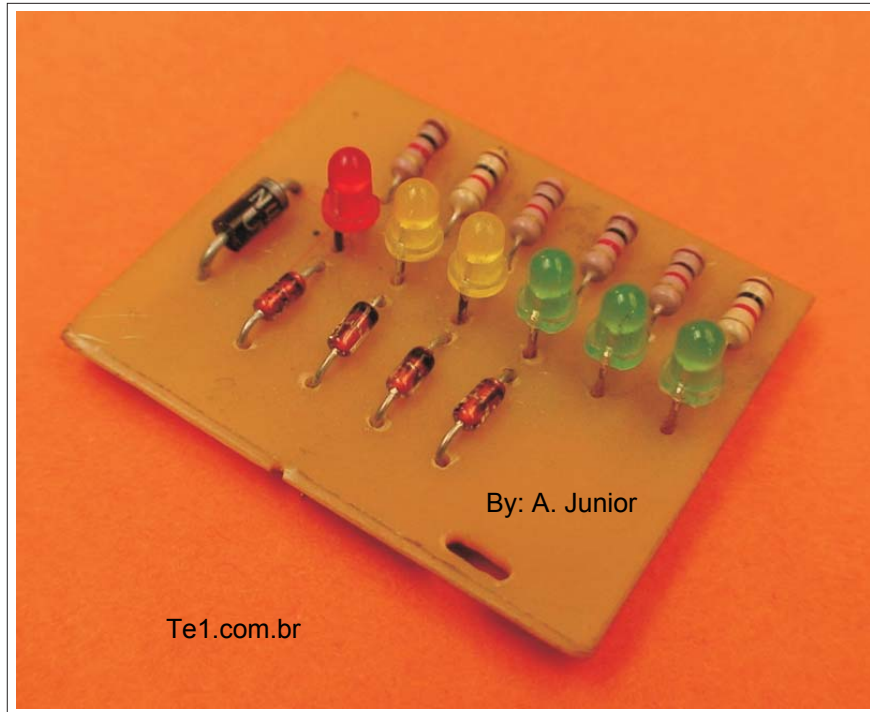



VU meter com 6 leds

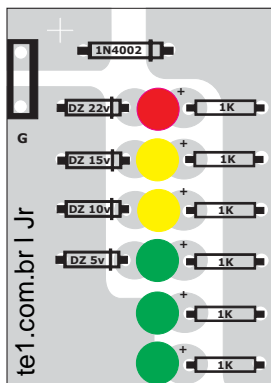


Obs :. O valor dos diodos zener variam conforme a potência do amplificador, leia o artigo.



Layout

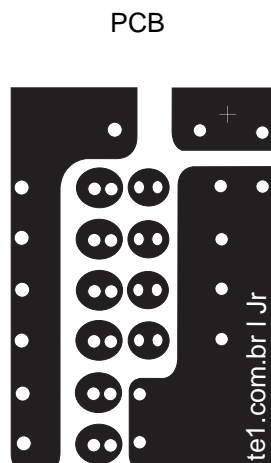

PCB

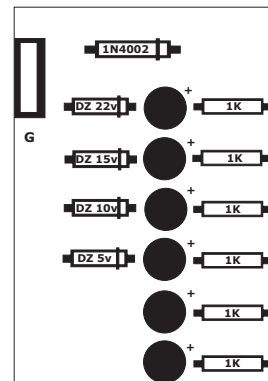

Silk-screen

Lista de Componentes :

- 6 resistores de 1K
- 6 leds
- 1 Diodo 1N4002
- 1 Diodo Zener de 5v
- 1 Diodo Zener de 10v
- 1 Diodo Zener de 15v
- 1 Diodo Zener de 22v